

A SG vol 3 EX 25.1 (Electro-motive force and Ohm's law)

The electrical resistivity of tungsten is  $53 \Omega\text{-m}$  (at  $20^\circ\text{C}$ )

The resistance  $R = \rho L/A$

- a) 28 gauge wire has a diameter of  $0.321\text{ mm}$

$$A = \pi (\frac{D}{2})^2 = 8.1 \times 10^{-8} \text{ m}^2$$

$$L = 1\text{ m}$$

$$R = 0.65 \Omega$$

$$I = V/R = 9/0.65$$

$$I = 13.8 \text{ Amps}$$

- b) If there are 2 wires, the area will be doubled, the resistance will be halved, and the current will be doubled. In other words, 13.8 amps will flow through each wire.
- c) If the wires are end-to-end (series) the length ( $L$ ) will be doubled; the resistance ( $R$ ) will be doubled, and the current ( $I$ ) will be halved. So 6.9 Amps will flow thru each wire.
- d) If the battery could not provide this much current, the voltage would drop to a level from which it could source its highest current level.