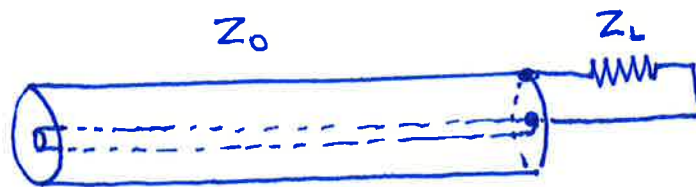


①

BB 5.2 (Transmission of energy down a coaxial cable.)

- In this problem, we will explore how the type of load (e.g. antenna, speaker, resistor, short) affects the transmission of energy down a particular RF transmission line: the coaxial cable.

- In particular, we will look at this situation:



- The coax has a characteristic impedance Z_0 . The load has impedance Z_L . We will consider 2 cases: $Z_L = Z_0$ and $Z_L = 0$. If $Z_L = Z_0$, the load is "impedance matched" to the coax, and there will be no reflected energy. If $Z_L = 0$, the inner & outer conductors are shorted, and the load will act like a mirror, reflecting all the energy sent down the coax.
- we will plot $S(z, t)$, the Poynting vector (in $\frac{\text{Watts}}{\text{m}^2}$) at various points along the coax for various times. (in each case).

- Generally speaking, there will be a traveling voltage (and current) wave propagating down the coax. There may also be a reflected voltage (and current) wave. So let's take

$$V(z,t) = \underbrace{V_i e^{i(\omega t - \beta z)}}_{\text{incident}} + \underbrace{V_r e^{i(\omega t + \beta z)}}_{\text{reflected}} \quad (\text{Eq. 5.46})$$

$$I(z,t) = I_i e^{i(\omega t - \beta z)} + I_r e^{i(\omega t + \beta z)}$$

- If we take the load to be at $z=0$, then we have

$$V_L = V(0,t) = (V_i + V_r) e^{i(\omega t)}$$

$$I_L = I(0,t) = (I_i + I_r) e^{i(\omega t)}$$

- The characteristic impedance of the transmission line is defined as the ratio of voltage to current

$$Z_0 \equiv \frac{V}{I}$$

- Using our voltage and current equations, and (Eqs 5.33), we can show that $I_i = \frac{V_i}{Z_0}$ and $I_r = \frac{-V_r}{Z_0}$. Thus

$$I_L = \left(\frac{V_i}{Z_0} + \frac{V_r}{Z_0} \right) e^{i\omega t}$$

- This gives $Z_L = \frac{V_L}{I_L} = Z_0 \left(\frac{V_i + V_r}{V_i - V_r} \right)$

Inverting gives

$$\boxed{\frac{V_r}{V_i} = \frac{Z_L - Z_0}{Z_L + Z_0}}$$

(Eq 5.49)

Similarly

$$\boxed{\frac{I_r}{I_i} = \frac{Z_0 - Z_L}{Z_0 + Z_L}}$$

(Eq 5.50)

- We can use eqs. 5.49 & 5.50 to find out the amplitude of the reflected voltage (or current) waves.

- If $Z_L = Z_0$ then $\frac{V_R}{V_i} = 0 \Rightarrow$ no reflected voltage

- $\frac{I_R}{I_i} = 0 \Rightarrow$ no reflected current

- So: our voltage and current in the coax look like

$$V(z,t) = V_i e^{i(\omega t - \beta z)}$$

$$I(z,t) = \left(\frac{V_i}{Z_0}\right) e^{i(\omega t - \beta z)}$$

- The Poynting vector $S(z,t) = \frac{\text{Power}(z,t)}{\text{area}}$ where

$$\text{Power: } P(z,t) = (\text{Re } V)(\text{Re } I) \quad (\text{Eqn. 5.42})$$

- This then becomes

$$P(z,t) = (V_i \cos(\omega t - \beta z)) \left(\frac{V_i}{Z_0} \cos(\omega t - \beta z)\right)$$


$$P(z,t) = \left(\frac{V_i^2}{Z_0}\right) \cos^2(\omega t - \beta z)$$

- What does this look like if the coax has a length of λ ?

$P(z,t)$ = power along coax

position of load

(4)

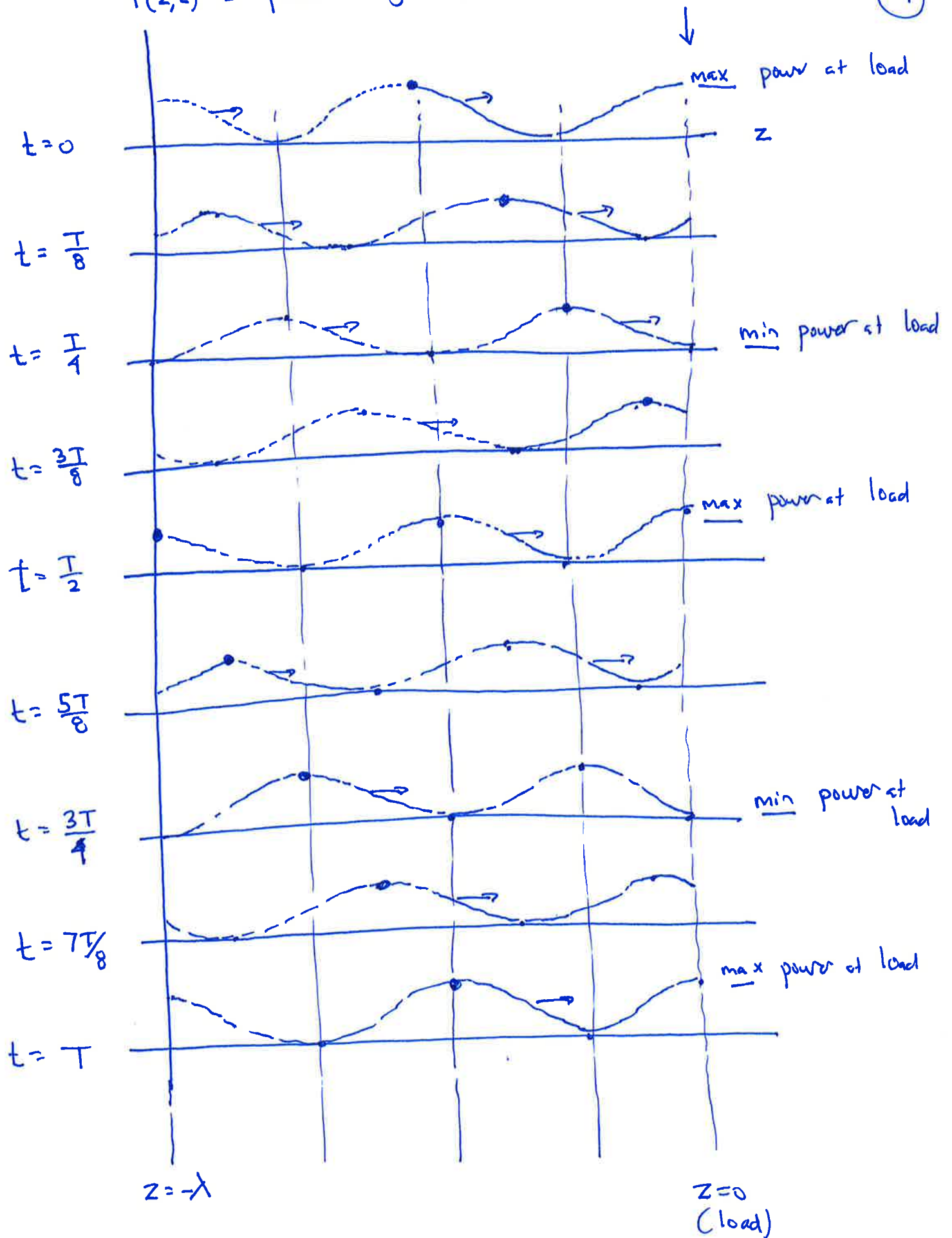

- The the power delivered to the load goes through two maxima every period. The time average power is just

$$\begin{aligned} \langle P(z=0) \rangle &= \frac{1}{T} \int_0^T P(z,t) dt \\ &= \frac{1}{T} \frac{V_i^2}{Z_0} \int_0^T \cos^2(\omega t) dt \\ \langle P(z=0) \rangle &= \frac{1}{2} \frac{V_i^2}{Z_0} \text{ watts} \end{aligned}$$

- But what if $Z_L = 0$? This means that the load is essentially a short circuit. No voltage can develop across the load. So $V_L = V(z=0,t) = 0$

Using our equations

$$\frac{V_r}{V_i} = \frac{Z_L - Z_0}{Z_L + Z_0} = -1$$

we see that $V_r = -V_i$ and that

$$\frac{I_r}{I_i} = \frac{Z_0 - Z_L}{Z_0 + Z_L} = 1$$

and $I_r = I_i$

(6)

• This means that

$$V(z,t) = V_i \left[e^{-ikz} - e^{+ikz} \right] e^{i\omega t}$$

$$I(z,t) = I_i \left[e^{-ikz} + e^{+ikz} \right] e^{i\omega t}$$

$$\rightarrow V(z,t) = -2i V_i e^{i\omega t} \left[\frac{e^{ikz} - e^{-ikz}}{2i} \right]$$

$$= -2i V_i \left[\cos(\omega t) + i \sin(\omega t) \right] \sin(kz)$$

$$= 2V_i \sin(kz) \left[\sin(\omega t) - i \cos(\omega t) \right]$$

$$\text{Re} [V(z,t)] = 2V_i \sin(kz) \sin(\omega t)$$

$$\rightarrow I(z,t) = 2I_i \cos(kz) \left[\cos(\omega t) + i \sin(\omega t) \right]$$

$$\text{Re} [I(z,t)] = 2I_i \cos(kz) \cos(\omega t)$$


• The instantaneous power is $P(z,t) = (\text{Re} V)(\text{Re} I)$

$$P(z,t) = 4V_i I_i \underbrace{\sin(kz) \cos(kz)}_{\frac{1}{2} \sin(2kz)} \underbrace{\sin(\omega t) \cos(\omega t)}_{\frac{1}{2} \sin(2\omega t)}$$

$$P(z,t) = V_i I_i \sin(2kz) \sin(2\omega t)$$

$$P(z,t) = \left(\frac{V_i^2}{Z_0} \right) \sin(2kz) \sin(2\omega t)$$

which is a standing wave.

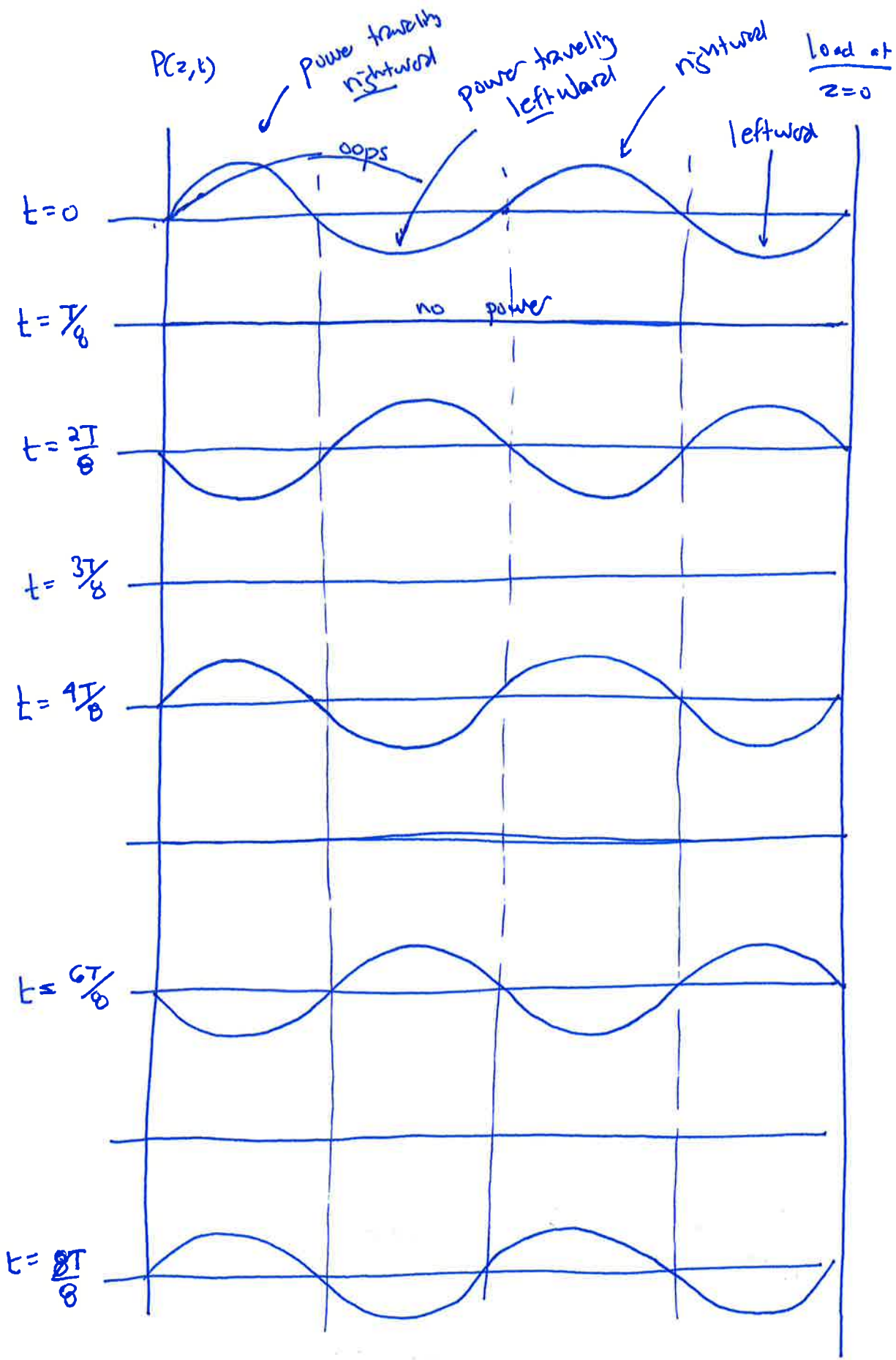

This is a standing wave in space and time.

There is no time average power transmission.

All incident energy is reflected.